

## Pire wheel


(i) current:

$$I = V / R$$

$$= P / V$$

$$= \sqrt{P / R}$$

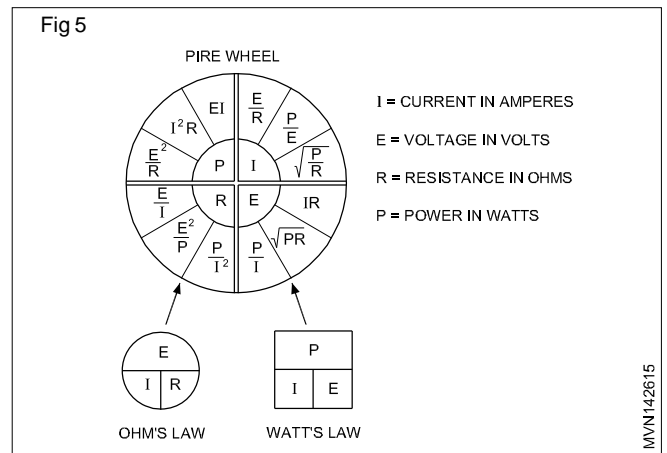The formulae (or equations) to solve for unknown voltage, current, resistance or power can be obtained by combining Ohm's law and Power law. This is shown in Fig.5



## Electrical measuring instruments and electrical circuits


**Objectives:** At the end of this lesson you shall be able to

- explain the connection of an ammeter in the circuit
- state the use of an ammeter
- explain the care to be taken of an ammeter
- explain the connection of a voltmeter
- explain the use of a voltmeter
- explain the care to be taken of voltmeters
- explain the connection of an ohmmeter
- state the use of an ohmmeter
- explain the care to be taken of ohmmeters
- explain the maintenance of meters
- state simple electric circuit
- state open electric circuit
- state short electric circuit
- state series circuits & parallel circuits
- list the types of resistance
- explain resistance symbols used in wiring diagram.

There are three basic types of meters used to test the electric circuit and accessories. The following meters are used in automobiles.

- Ammeter
- Voltmeter
- Ohmmeter

**Ammeter** (Fig 1)

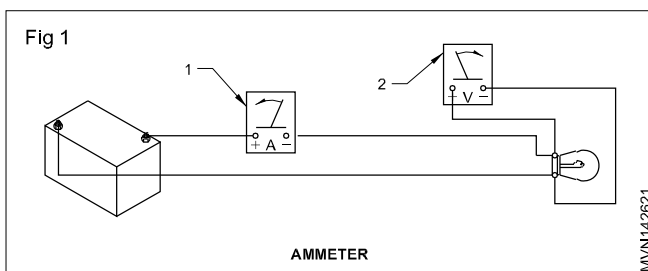

The ammeter (1) is fitted on the vehicle panel board/ dashboard.

It is connected in series in the circuit as shown in the fig.1.

### Uses of ammeter

An ammeter is used to measure the amount of current flowing in the circuit.

This is connected in series with the load.

It is used to indicate the rate at which the battery is being charged or discharged.

### Care

Do not connect an ammeter in parallel in the circuit.

Take care of "+" and "-" mark on terminals.

Use DC meter for automobile charging system.

Select and use an ammeter as per the required range.

### Voltmeter

A voltmeter (2) is used to measure electrical voltage. It is not fitted permanently on the vehicle but used separately whenever required. It is connected in parallel with the circuit. Use DC voltmeter for automobiles.

### Uses of a voltmeter

To measure the voltage at any point of circuit.

To measure the voltage drop in the circuit.


To check the condition of the battery.

### Care

Select the voltmeter as per the required range.

Do not connect the voltmeter in series in the circuit.

## Ohmmeter (Fig 2)

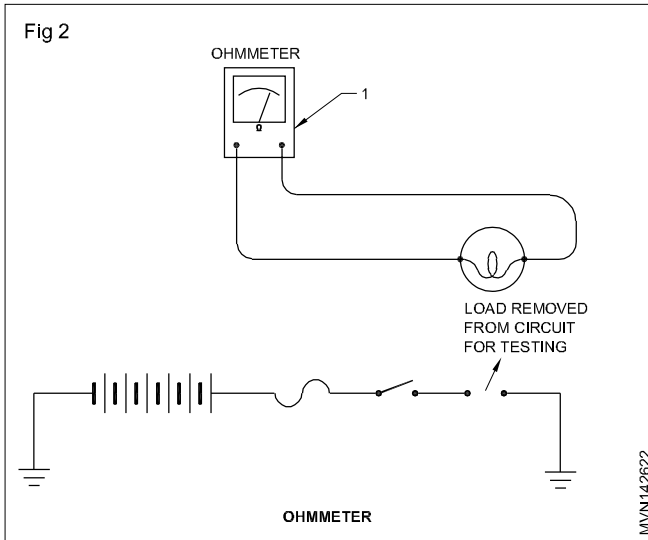

An ohmmeter (1) is also known as resistance meter.

It is not fitted permanently on the vehicle but is used separately whenever required.

It has its own built-in power source. Hence the device/circuit being checked with the ohmmeter should be disconnected from the power supply as shown in the figure, to prevent damage to the ohmmeter.

The unit of resistance is an ohm.

### Uses of ohmmeter

An ohmmeter is used:

- to measure the resistance of any conductor
- to measure the resistance of any load
- to check the continuity of the field coils.

### Care

Do not connect an ohmmeter to any part of a live circuit.

Do not connect an ohmmeter across the terminals of a battery.

### Maintenance of meters

Handle the meters with care.

Keep the connections tight while the meters are in use.

Use the meters within specified loads.


After use, keep the meters in a separate place.

### Electrical circuits

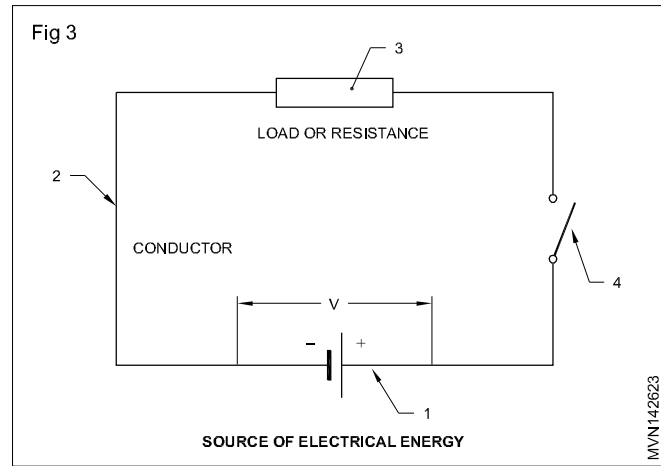
#### Simple electrical circuit (Fig 3)

A simple electric circuit is a complete pathway of the current flow from the battery via the switch and load and back to the battery. An electric circuit consists of :

- a voltage source (1)
- connecting wires (conductors) (2)
- a load (lamp or motor) (3)
- switch (4).




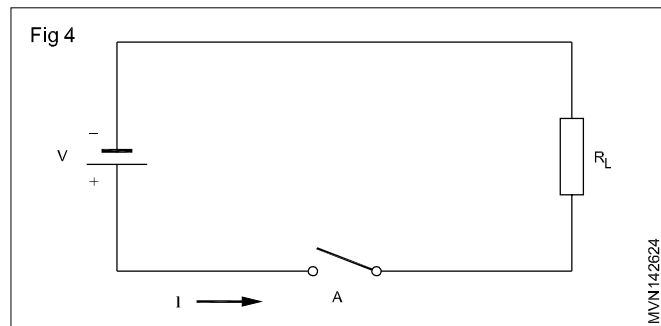**Open circuit (Fig 4):** In an open circuit, an infinite resistance is provided, most of the time by the open switch (A). Therefore no current can flow.



**Short circuit :** A short circuit will occur when two terminals of the same circuit touch each other. A short circuit may also occur if the insulation between the two cores of the cable are defective. This results in a lower resistance. This causes a large current to flow which can become a hazard.

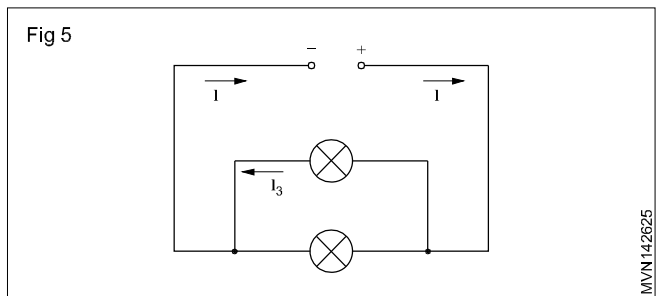**Parallel circuit (Fig 5):** In this circuit two or more loads are connected. Each load is provided with its own path to the source of supply.



#### Example

A pair of head lights is connected in parallel circuit. When wired in parallel the failure of one bulb will not effect the operation of the other bulb. Each load receives full system voltage.

The formula to calculate resistance in a parallel circuit is:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

where

$I$  = current  
 $R$  = resultant resistance  
 $R_1, R_2, R_3$  = resistance of each load.

**Series circuit :** This circuit consists of only one load and one source of supply. It has one continuous path for the flow of current. Hence the current flows through all the load in a sequence in circuit. If any of the parts fails the circuit breaks and the current stops flowing. If three resistances  $R_1, R_2, R_3$  are connected in series then the total resistance  $R$  is given by the formula  $R = R_1 + R_2 + R_3$ .

$$\text{Resistance}(R) = \frac{\text{Voltage}(V)}{\text{Current}(I)}$$

$$\text{Current}(I) = \frac{\text{Voltage}(V)}{\text{Resistance}(R)}$$

$$\text{Voltage} = \text{Current}(I) \times \text{Resistance}(R)$$

### TYPES OF RESISTANCE

Based on the ohmic value of resistance it is grouped as low, medium and high resistance.

#### Low resistance

Range : 1 Ohm and below.  
 Uses : Armature winding, ammeter.


#### Medium resistance

Range : Above 1 Ohm up to 1,00,000 Ohm.  
 Uses : Bulbs, heaters, relay starters.
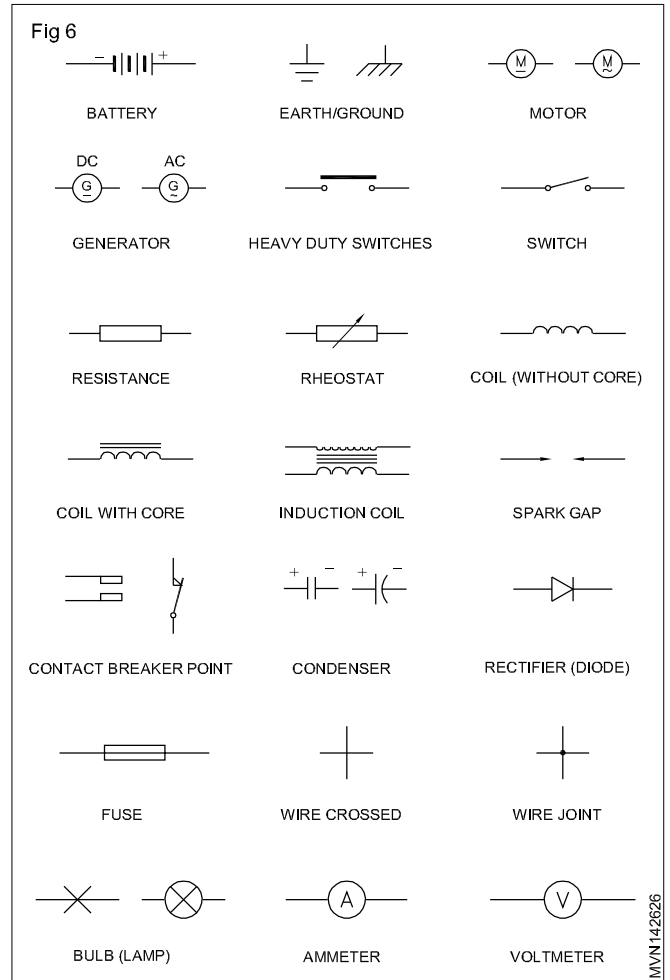
#### High resistance

Range : Above 1,00,000 Ohm (100 k.Ohms).  
 Use : Lamps.

**Electrical symbols used in a wiring diagram (Fig 6):** Automotive circuits are generally shown by wiring diagrams. The parts in those diagrams are represented by symbols. Symbols are codes or signs that have been adopted by various automobile manufacturers as a convention.



## Multimeter

**Objectives:** At the end of this lesson you shall be able to

- state the function of multimeter controls
- explain about the dial (scale) of the multimeter
- explain about zero adjustment during ohmmeter function
- state the function of digital multimeter
- state the application of the multimeter
- state the precautions to be followed while using a multimeter.

A multimeter is an instrument in which the functions of an ammeter, voltmeter and ohmmeter are incorporated for measurement of current, voltage and resistance respectively. Some manufacturers call this a VOM meter as this meter is used as volt, ohm and milli ammeter, Multimeters use the basic d'Arsonval (PMMC) movement for all these measurements. This meter has facilities through various switches to change the internal circuit to

convert the meter as voltmeter, ammeter or ohmmeter.

There are two major types of multimeters

- i Ordinary multimeters having passive components.
- ii Electronic multimeters having active and passive components. An electronic multimeter may be of the analog type or digital type.


Most of the ordinary multimeters will have a sensitivity of 20k ohms per volt in the voltmeter mode whereas electronic multimeters have internal resistances to the tune of 5 to 10 megohms, irrespective of the selected voltage range.

There are several types of multimeters available in the market, manufactured by various manufactures. Each model differs from the others by the extra facilities available. It is a versatile tool for all automobile. With proper usage and care, it could give service for many years.

Rectifiers are provided inside the meter to convert AC to DC in the AC measurement circuit.
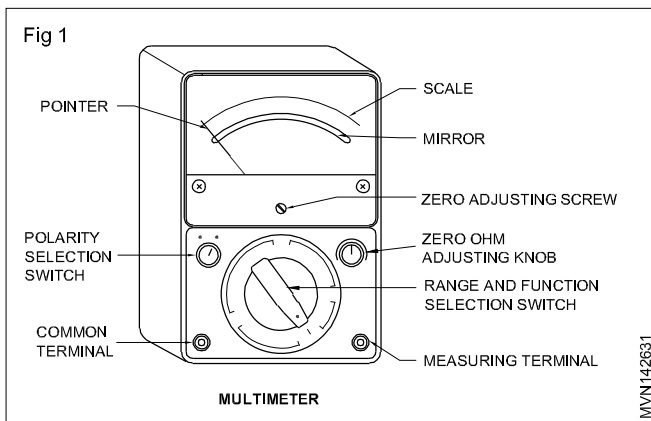
### Parts of a multimeter

A standard multimeter consists of these main parts and controls as shown in Fig 1.




### Scale of multimeter

Separate scales are provided for:

- resistance
- voltage and current.

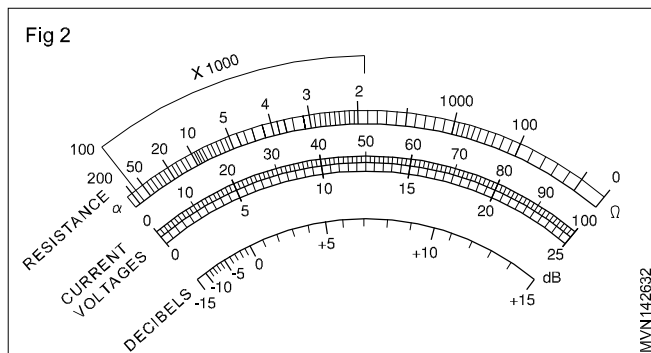The scale of current and voltage are uniformly graduated (Fig 2)



The scale for resistance measurement is non-linear. That is, the divisions between zero and infinity (∞) are not equally spaced. As you move from zero to the left across the scale, the division become closer together.

The scale is usually 'backward', with zero at the right.

### Zero adjustment

When the selector switch is in the resistance range and the leads are open, the pointer is at left side of scale, indicating infinite (∞) resistance (open circuit). When the leads are shorted, the pointer is at right side of the scale, indicating zero resistance.


The purpose of the zero ohm adjusting knob is to vary the variable resistor and adjust the current so that the pointer is at exactly zero when the leads are shorted. It is used to compensate for changes in the internal battery voltage due to aging.

### Multiple range

Shunt (parallel) resistors are used to provide multiple ranges so that the meter can measure resistance values from very small to very large values. For each range, a different value of shunt resistance is switched on. The shunt resistance increases for the higher ohm ranges and is always equal to the centre scale reading on any range. These range settings are interpreted differently from those of the ammeter or voltmeter. The reading on the ohmmeter scale is multiplied by the factor indicated by the range setting.
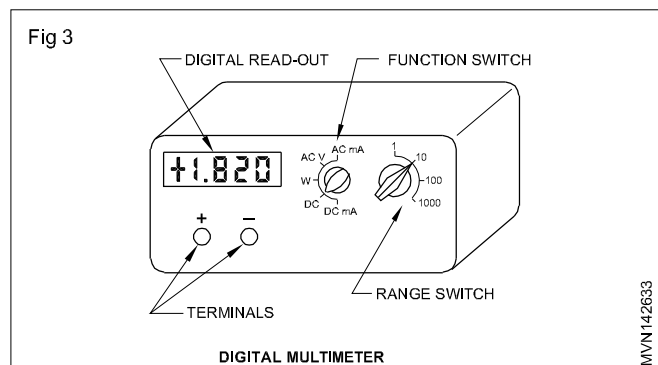
### Digital multimeter (DMM)

In a digital multimeter the meter movements is replaced by a digit read - out. (Fig 3) this read-out is similar to that used in electronic calculators. The internal circuitry of the digital multimeter is made up of digital integrated circuits. Like the analog-type multimeter, the digital multimeter has also a front panel switching arrangement. The quantity measured is displayed in the form of a four digit number with a properly placed decimal point. When d quantities are measured, the polarity is identified by means of a + or - sign displayed to the left of the number.



**Remember, when a multimeter is set for the ohmmeter function, the multimeter must not be connected to the circuit with the circuit's power is on.**

# Resistors

**Objectives:** At the end of this lesson you shall be able to

- name the types of resistors, construction and power rating
- state the meaning of tolerance in resistor
- find the value of a resistor using colour code
- state the application and types of resistor leads.

## Fixed value resistors

Its ohmic value is fixed. This value cannot be changed by the user. Resistors of standard fixed values are manufactured for use in majority of applications.


Fixed resistors are manufactured using different materials and by different methods. Based on the material used and their manufacturing method/process, resistors carry different names.

Fixed value resistors can be classified based on the type of material used and the process.

## Carbon composition resistors
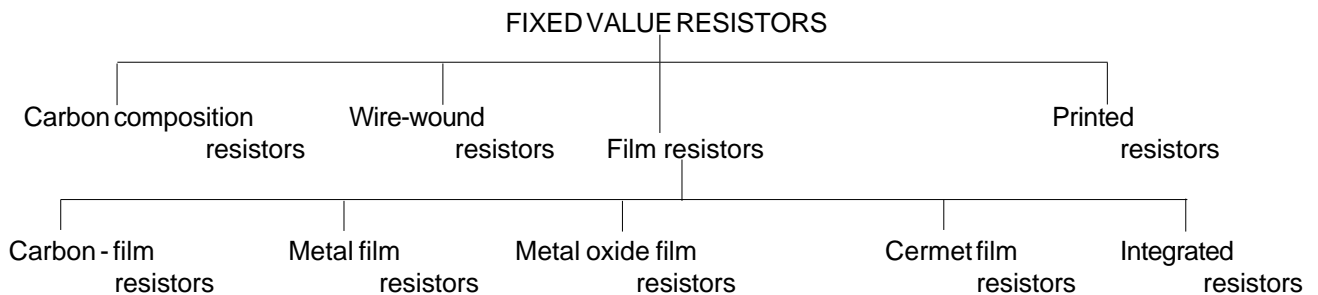
### Construction


These are the simplest and most economical of all other types. Brief constructional detail of the simplest type of carbon composition resistors commonly called carbon resistor.




A mixture of finely powdered carbon or graphite(A), filler and binder is made into rods or extruded into desired shapes. Leads(B) made of tinned copper are then attached to the body either by soldering or embedding(C) in the body. A protective layer/tube(D) of phenolic or Bakelite is moulded around the assembly. Finally its resistance value is marked on the body.
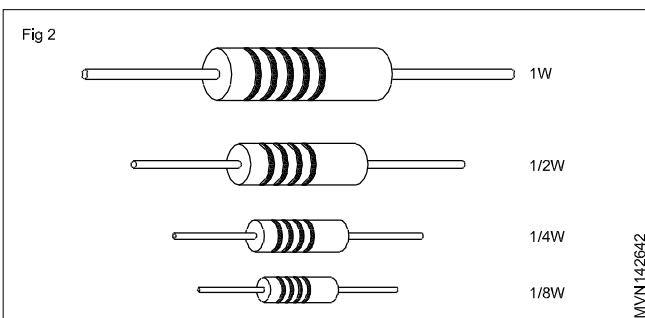
## Resistor values - coding schemes (Fig.1)

For using resistors in circuits, depending upon the type of circuit in which it is to be used, a particular type, value and wattage of resistor is to be chosen. Hence before using a resistor in any circuit, it is absolutely necessary to identify the resistor's type, value and power rating.



Selection of a particular type of resistor is possible based on its physical appearance. Table 1 at the end of this lesson illustrates the physical appearance of most commonly used fixed value resistors. The resistance value of a resistor will generally be printed on the body of the resistor either directly in ohms as shown in Fig 2a or using a typographic code as shown in Fig 2b or using a colour code as shown in Fig 2c.

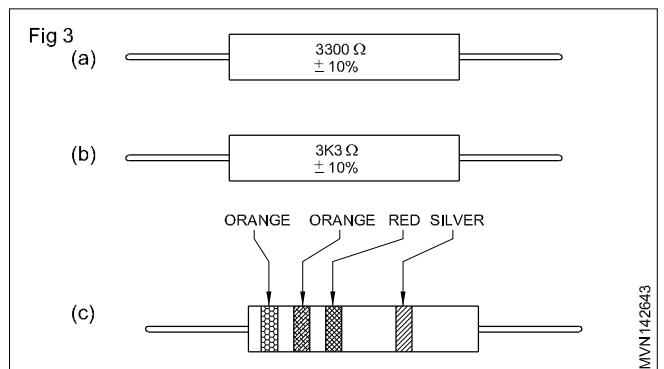

## Colour band coding of resistors

Colour band coding as shown in Fig 2c is most commonly used for carbon composition resistors. This is because the physical size of carbon composition resistor is generally small, and hence, printing resistance values directly on the resistor body is difficult. Refer Table 1.

## Tolerance

In bulk production/ manufacturing of resistors, it is difficult and expensive to manufacture resistors of particular exact values. Hence the manufacturer indicates a possible variation from the standard value for which it is manufactured. This variation will be specified in percentage tolerance. Tolerance is the range(max-to-min) within which the resistance value of the resistor will exist.

## Applications

Carbon composition, fixed value resistors are the most widely used resistors in general purpose electronic circuits such as radio, tape recorder, television etc. More than